



QP CODE: 4205 (CBCS)

43

PITHAPUR RAJAH'S GOVERNMENT COLLEGE (AUTONOMOUS), KAKINADA  
IV -SEMESTER END EXAMINATIONS-MARCH-2020

II YR B.Sc., SUBJECT/ PAPER: ELECTRONICS

OP-AMP & DIGITAL IC APPLICATIONS

DATE: 01.04.2020(WEDNESDAY), TIME: 09.00 AM

Max. Marks: 60

Reg. No.

Duration: 2½ Hrs

SECTION – A

Answer any three questions.

2x10=20  
3x10=30M

1. Draw the circuit diagram of Inverting amplifier and explain their operation.
2. Explain the working and construction of sine wave generator using op-amp.
3. Explain the pin diagram of IC – 555 timer.
4. What is counter? Design and explain mod 16 counter.
5. Explain the working of A/D converter.

SECTION – B

Answer any Five Questions.

6x5=30M

6. How does op-amp act as a voltage follower?
7. Calculate the output voltage of an op-amp summing amplifier for the following set of voltages and resistors.  $R_f=10k\Omega$ ,  $v_1=6V$ ,  $v_2=3V$ ,  $v_3=0.8V$ ,  $R_1=10k\Omega$ ,  $R_2=5k\Omega$ ,  $R_3=6k\Omega$ .
8. An Inverting amplifier has  $R_1=10k\Omega$ ,  $R_f=125k\Omega$ . Find the output voltage, the input resistance and input current for an input voltage 4 volt.
9. Explain the working of op-amp as comparator.
10. Write a short note on astable multivibrator using IC 555 timer.
11. Draw and explain BCD to decimal decoder (IC7442).
12. Explain how op-amp as low pass filter.
13. Explain successive approximation of ADC.
14. Give brief explanation of single slope ADC.